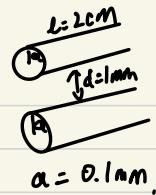




Q1

- 1) Two parallel wires of radius  $a = 0.1\text{ mm}$  and length  $2\text{ cm}$  separated by a distance  $d = 1\text{ mm}$  connect two elements on the motherboard of a computer. The wires are assumed to be made of perfect electric conductors and reside in a lossless medium with permittivity  $\epsilon = 2\epsilon_0$  and permeability  $\mu_0$ .

- a) Consider two signals: One of frequency  $1\text{ GHz}$  and the other of frequency  $20\text{ GHz}$ . Do we have to consider the two wires as a transmission line for the first signal? Do we have to consider the two wires as a transmission line for the second signal?
- b) In the case we have to consider the wires as a transmission line, what are the characteristic impedance and propagation constant of the line?



$$a) \quad l \ll CT$$

$$f = 1\text{ GHz} \Rightarrow T = 10\text{ ns}$$

$$f = 20\text{ GHz} \Rightarrow T = 50\text{ ps}$$

$$\text{Signal 1: } 10\text{ ns} \cdot 3 \cdot 10^8 \frac{\text{m}}{\text{s}} = 3\text{ m}$$

$$\text{Signal 2: } 50\text{ ps} \cdot 3 \cdot 10^8 \frac{\text{m}}{\text{s}} = 0.015\text{ m} = 1.5\text{ cm}$$

For Signal 1  $l = 2\text{ cm} \ll CT = 3\text{ m}$ , so we don't have to consider it as Transmission line

For Signal 2  $l > CT \therefore$  we consider it as Transmission line

$$b) \quad \epsilon = 2\epsilon_0 = 8.85 \cdot 10^{-12} \cdot 2$$

Since wire made of perfect electric conductors and reside in a lossless medium  
 $R'$  and  $G'$  is 0



(b) Two-wire line

$$R_s = \sqrt{\frac{\pi f \mu_0}{\sigma_c}} \quad (\Omega)$$

Two Wire	
$\frac{R_s}{\pi a}$	$= R'$
$\frac{\mu}{\pi} \ln \left[ (d/2a) + \sqrt{(d/2a)^2 - 1} \right]$	$= L'$
$\frac{\pi \sigma}{\ln \left[ (d/2a) + \sqrt{(d/2a)^2 - 1} \right]}$	$= G'$

$$R_s = \sqrt{\frac{\pi f \mu_0}{\sigma_c}} \quad (\Omega) \quad L' = \frac{\mu_0}{\pi} \left( \ln \left[ \frac{1}{0.2} \right] + \sqrt{\left( \frac{1}{0.2} \right)^2 - 1} \right)$$

$$C' = \frac{\pi \epsilon}{\ln \left[ \left( \frac{1}{0.2} \right) + \sqrt{\left( \frac{1}{0.2} \right)^2 - 1} \right]}$$

$$d = 1 \text{ mm}$$

$$a = 0.1 \text{ mm}$$

$R'$  and  $G'$  is 0

$$x = \ln \left[ \frac{d}{2a} + \sqrt{\left( \frac{d}{2a} \right)^2 - 1} \right]$$

$$Z_0 = \sqrt{\frac{j\omega L'}{j\omega C'}} = \sqrt{\frac{L'}{C'}} = \sqrt{\frac{1/x}{\pi} \cdot \frac{x}{\pi \cdot 2\epsilon_0}}$$

$$\epsilon_r = \frac{\epsilon}{\epsilon_0}$$

= 2

$$u_0 = 4\pi \cdot 10^7$$

$$= \sqrt{\frac{u_0}{2\epsilon_0} \cdot x^2 \cdot \frac{1}{\pi^2}}$$

$$= \underbrace{\sqrt{\frac{u_0}{2\epsilon_0} \cdot \frac{1}{\pi}}} \cdot \underbrace{\ln \left( \frac{d}{2a} + \sqrt{\left( \frac{d}{2a} \right)^2 - 1} \right)}_{84.814 \quad 2.292}$$

$$= 194.43 \Omega$$

Propagation Constant

Characteristic Impedance.

Lossless  
two wire

$$\alpha = 0, \beta = \omega \sqrt{\epsilon_r} / c$$

$$u_p = c / \sqrt{\epsilon_r} \quad Z_0 = \left( 120 / \sqrt{\epsilon_r} \right) \cdot \ln \left[ (d/2a) + \sqrt{(d/2a)^2 - 1} \right]$$

$$Z_0 \approx \left( 120 / \sqrt{\epsilon_r} \right) \ln(d/a), \text{ if } d \gg a$$

$$\gamma = 0 + j \frac{\omega \sqrt{\epsilon_r}}{c}$$

$$Z_0 \approx \frac{120}{\sqrt{\epsilon_r}}$$

$$\omega = 2\pi \cdot 20 \text{ G} = 1.26 \cdot 10^9 \text{ Hz}$$

$$\beta = \frac{\omega \cdot \sqrt{2}}{3 \cdot 10^8} = 592.38$$

$$\gamma = 0 + j 592.38$$

Q2

2)

- 2.10** Using a slotted line, the voltage on a lossless transmission line was found to have a maximum magnitude of 1.5 V and a minimum magnitude of 0.6 V. Find the magnitude of the load's reflection coefficient.

Reflection coefficient is the ratio between

$$\Gamma = \frac{V_0^-}{V_0^+} = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{Z_L/Z_0 - 1}{Z_L/Z_0 + 1} \quad (\text{dimensionless})$$

Voltage standing wave ratio:

$$S = \frac{|V|_{\max}}{|V|_{\min}} = \frac{1 + |\Gamma|}{1 - |\Gamma|} \quad (\text{dimensionless})$$

$$\frac{1.5}{0.6} = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$

$$\Rightarrow \frac{5}{2} - \frac{5}{2}|\Gamma| = 1 + |\Gamma|$$

$$\frac{3}{2} = \frac{7}{2}|\Gamma|$$

$$|\Gamma| = \frac{3}{7}$$

3)

**2.12** A 50- $\Omega$  lossless transmission line is terminated in a load with impedance  $Z_L = (30 - j50) \Omega$ . The wavelength is 8 cm. Find the following:

- (a) The reflection coefficient at the load.
- (b) The standing-wave ratio on the line.
- (c) The position of the voltage maximum nearest the load.
- (d) The position of the current maximum nearest the load.

$$Z_0 = 50 \Omega$$

$$Z_L = 30 - j50$$

$$\begin{aligned} a) \quad \Gamma &= \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{30 - j50 - 50}{80 - j50} = 0.1011 - j0.5618 \\ &= \boxed{0.5708 \angle -79.796^\circ} \end{aligned}$$

b)

**Voltage standing wave ratio:**

$$S = \frac{|\tilde{V}|_{\max}}{|\tilde{V}|_{\min}} = \frac{1+|\Gamma|}{1-|\Gamma|} \quad (\text{dimensionless})$$

$$S = \frac{1 + 0.5708}{1 - 0.5708} \approx \boxed{3.66}$$

c)

First maximum

$$\begin{aligned} \theta_r \geq 0, \quad &\Rightarrow l_{\max} = \theta_r \lambda / 4\pi \quad (\text{for } n=0) \\ \theta_r < 0, \quad &\Rightarrow l_{\max} = (\theta_r \lambda / 4\pi) + \lambda / 2, \quad (\text{for } n=1) \end{aligned}$$

$$\begin{aligned} l_{\max} &= \frac{\theta_r \lambda}{4\pi} + \frac{\lambda}{2} \\ &= \frac{-79.796\pi}{180} \cdot 0.08 + \frac{0.08}{2} \end{aligned}$$

$$= -8.8662 \cdot 10^{-3} + 0.04$$

$$l_{\max} \approx 0.031 \text{ m} = 3.1 \text{ cm}$$

d)

First minimum

$$l_{\min} = \begin{cases} l_{\max} + \lambda/4, & \text{if } l_{\max} < \lambda/4, \\ l_{\max} - \lambda/4, & \text{if } l_{\max} \geq \lambda/4. \end{cases}$$

$$\frac{\lambda}{4} = 0.02 \text{ m} \leq l_{\max}$$

$$l_{\min} = l_{\max} - \frac{\lambda}{4}$$

$$= 0.011 \text{ m}$$

$$= \boxed{1.1 \text{ cm}}$$

Q4

4)

**2.13\*** On a  $150\Omega$  lossless transmission line, the following observations were noted: distance of first voltage minimum from the load = 3 cm; distance of first voltage maximum from the load = 9 cm;  $S = 3$ . Find  $Z_L$ .

$$S = \frac{1 + |r|}{1 - |r|} = 3$$

$$\begin{aligned} 3 - 3|r| &= 1 + |r| \\ 2 &= 4|r| \\ |r| &= 0.5 \end{aligned}$$

$$l_{\max} = \frac{\theta_r \lambda}{4\pi} + \frac{\lambda}{2}$$

$$l_{\min} = l_{\max} - \frac{\lambda}{4}$$

$$l_{\min} = l_{\max} - \frac{\lambda}{4}$$

$$3 = 9 - \frac{\lambda}{4}$$

$$\frac{\lambda}{4} = 6$$

$$\lambda = 24 \text{ cm}$$

$$\frac{l_{\max} \cdot 4\pi}{\lambda} = \theta_r$$

$$\frac{0.09 \cdot 4\pi}{0.24} = \theta_r$$

$$\theta_r = \frac{3}{2}\pi$$

$$\begin{aligned} r &= 0.5 \angle \frac{3}{2}\pi \\ &= 0 - j0.5 \end{aligned}$$

$$r = \frac{Z_L - 150}{Z_L + 150}$$

$$Z_L = 90 - 120j$$

$$\begin{aligned} -0.5i &\times -75j = x - 150 \\ x(-1 - 0.5j) &= -150 + 75j \\ x &= \frac{-150 + 75j}{-1 - 0.5j} \\ &= \frac{112.5 - 150j}{1.25} \end{aligned}$$

$$(-150 + 75j)(-1 + 0.5j)$$

$$\begin{aligned} 150 - 75j &- 75j - 37.5 \\ 112.5 - 150j & \end{aligned}$$

- 5) (Quiz 1, Winter 2008) You are given a coaxial transmission line made of perfect electrically conducting cylinders of radii  $r_1 = 1 \text{ cm}$  and  $r_2 = 1.5 \text{ cm}$ . The space between the cylinders is filled with a material having the permittivity  $\epsilon = 4\epsilon_0$ , permeability  $\mu_0$ , and conductivity  $\sigma = 0$ . The transmission line is terminated by a load  $Z_L$  at  $z = 0$ . The transmission line is excited by a source of frequency  $f = 1.8 \text{ GHz}$ .

- a) Find parameters characterizing the transmission line, i.e.  $R', L', G', C', \beta, Z_0, \lambda, u_p$ .
- b) The magnitude and phase of the voltage measured at  $z_1 = 0$  and  $z_2 = -3 \text{ cm}$  are  $|\tilde{V}(0)| = 3 \text{ V}$ ,  $\arg(\tilde{V}(0)) = 0$  and  $|\tilde{V}(z_2)| = 2 \text{ V}$ ,  $\arg(\tilde{V}(z_2)) = \pi/3$ , respectively.
- Give expressions describing the voltage and current in the transmission line in the form of phasors and in the time domain representation.
- Find the reflection coefficient from the load  $Z_L$ .

Parameter	Coaxial
$R'$	$\frac{R_a}{2\pi} \left( \frac{1}{a} + \frac{1}{b} \right)$
$L'$	$\frac{\mu}{2\pi} \ln(b/a)$
$G'$	$\frac{2\pi\sigma}{\ln(b/a)}$
$C'$	$\frac{2\pi\epsilon}{\ln(b/a)}$

a)

The transmission line made of perfect electrically conducting

$$\text{So } R' = 0$$

$$L' = \frac{u_0}{2\pi} \ln \frac{r_2}{r_1} \quad u_0 = 4\pi \cdot 10^{-7} \text{ NA}^2$$

$$= 8.109 \cdot 10^{-8} \frac{\text{H}}{\text{m}}$$

$$G' = \frac{2\pi\sigma}{\ln(\frac{b}{a})} = 0 \quad b = 0$$

$$C' = \frac{2\pi\epsilon}{\ln(\frac{b}{a})}$$

$$= 5.486 \cdot 10^{-10} \frac{\text{F}}{\text{m}}$$

$$\epsilon_0 = 8.85 \cdot 10^{-12} \text{ F m}^{-1}$$

$$\epsilon = 3.54 \cdot 10^{-11} \text{ F m}^{-1}$$

$$\epsilon_r = \frac{\epsilon}{\epsilon_0}$$

	Propagation Constant $\gamma = \alpha + j\beta$	Phase Velocity $u_p$	Characteristic Impedance $Z_0$
General case	$\gamma = \sqrt{(R' + j\omega L')(G' + j\omega C')}$	$u_p = \omega/\beta$	$Z_0 = \sqrt{\frac{(R' + j\omega L')}{(G' + j\omega C')}}$
Lossless ( $R' = G' = 0$ )	$\alpha = 0, \beta = \omega\sqrt{\epsilon_r}/c$	$u_p = c/\sqrt{\epsilon_r}$	$Z_0 = \sqrt{L'/C'}$

$$\omega = 2\pi f = 1.13 \cdot 10^{10} \text{ Hz}$$

$$\beta = \omega \frac{\sqrt{\epsilon_r}}{c} = \omega \sqrt{L' C'} = \omega \sqrt{\mu \epsilon}$$

$$= 75.433$$

$$Z_0 = \sqrt{\frac{L'}{C'}} = 12.16 \Omega \quad \lambda = \frac{c}{f} = \frac{1}{6} \text{ m}$$

$$u_p = \frac{1}{\sqrt{L' C'}} = \frac{1}{\sqrt{L' C'}} = 1.5 \cdot 10^8 \frac{\text{m}}{\text{s}}$$

3. The voltage and current in phasor forms:  $\tilde{V}(z) = \tilde{V}^+ e^{-j\beta z} + \tilde{V}^- e^{j\beta z}$  and  $\tilde{I}(z) = (\tilde{V}'(z) = \tilde{V}^+ e^{-j\beta z} - \tilde{V}^- e^{j\beta z}) / Z_0$ . In the time domain,  $V(z, t) = |\tilde{V}^+| \cos(\alpha z - \beta z + \phi^+) + |\tilde{V}^-| \cos(\alpha z + \beta z + \phi^-)$  and  $I(z, t) = (|\tilde{V}'^+| \cos(\alpha z - \beta z + \phi^+) - |\tilde{V}'^-| \cos(\alpha z + \beta z + \phi^-)) / Z_0$

b) The magnitude and phase of the voltage measured at  $z_1 = 0$  and  $z_1 = -3\text{cm}$  are  $|\tilde{V}(0)| = 3V$ ,  $\arg(\tilde{V}(0)) = 0$  and  $|\tilde{V}(z_1)| = 2V$ ,  $\arg(\tilde{V}(z_1)) = \pi/3$ , respectively.

- Give expressions describing the voltage and current in the transmission line in the form of phasors and in the time domain representation.
- Find the reflection coefficient from the load  $\Gamma$ .

at  $z_1 = 0$

$$\tilde{V}(0) = V^+ e^0 + V^- e^0$$

$$3 = V^+ + V^- \Rightarrow V^+ = 3 - V^-$$

at  $z_2 = -3$

$$\tilde{V}(-3) = V^+ e^{-j(3\beta)} + V^- e^{j(3\beta)}$$

$$\tilde{V}(-3) = (3 - V^-) e^{j3} + V^- e^{-j3}$$

$$\tilde{V}_2 = 3 e^{j3} - V^- (e^{j3} - e^{-j3})$$

$$-\frac{\tilde{V}_2 - 3 e^{j3}}{e^{j3} - e^{-j3}} = V^- = \frac{2 e^{j3} - 3 e^{j3}}{e^{j3} - e^{-j3}}$$

Phasor

$$V^- = -4.6368 + j 14.066$$

$$V^+ = 3 - V^-$$

$$= 3 - (-4.6368 + j 14.066) = 7.6368 - j 14.066$$

$$\tilde{V} = (7.6368 - j 14.066) e^{j\beta z_2} + (-4.6368 + j 14.066) e^{-j\beta z_2}$$

$$\tilde{I} = \frac{V^+}{Z_0} e^{-j\beta z_2} + \frac{-V^-}{Z_0} e^{j\beta z_2}$$

$$= (0.628 - j 1.156) e^{-j\beta z_2} - (-0.3813 + j 1.156) e^{j\beta z_2}$$

Time Domain

$$v(z, t) = 16 \cos(\omega t - \beta z + [-1.0734]) + 14.8 \cos(\omega t - \beta z + 1.8892)$$

$$I(z, t) = 1.3162 \cos(\omega t - \beta z - 1.0734) + 1.218 \cos(\omega t - \beta z + 1.8892)$$

$$\Gamma = \frac{\bar{V}_o^-}{\bar{V}_o^+} = \frac{-4.6368 + j14.066}{7.6368 - j14.066} = \boxed{-0.9106 + j0.1647}$$

$$Z_L = \frac{\tilde{V}(0)}{\tilde{I}(0)} = \frac{3}{0.628 - j1.1567 + 0.3813 - j1.1567}$$
$$= \boxed{0.4753 + j1.0894}$$

c)

- c) Assume that the line is terminated by a load that is comprised of a resistor  $R_L$ , capacitor  $C_L$ , and inductor  $L_L$  connected in series. The values of  $R_L$ ,  $C_L$ , and  $L_L$  are finite. Find a combinations of  $R_L$ ,  $C_L$ , and  $L_L$  that leads to a matched load for the frequency  $f = 1.8 \text{ GHz}$  and to the VSWR=2 for the frequency  $f = 1.85 \text{ GHz}$  (please, give expressions/explanations before proceeding with calculating the numerical values of the result).

$$Z_L = Z_0 \\ = 12.16 \Omega$$

$$Z_L = R_L + j\omega L_L + \frac{1}{j\omega C_L} \quad \omega = 2\pi \cdot 1.8 \text{ G}$$

$$f = 1.8 \text{ GHz} \quad \text{Matched Load:}$$

$$Z_L = R_L = Z_0 \quad \text{and} \quad j\omega L_L + \frac{1}{j\omega C_L} = 0 \\ R_L = 12.16 \Omega \quad (j\omega)^2 \cdot L_L C_L + 1 = 0$$

$$-\omega^2 L_L C_L = -1$$

$$\omega^2 L_L C_L = 1$$

$$\text{Perfect matching} \quad \leftarrow L_L C_L = \frac{1}{\omega^2}$$

$$L_L C_L = 7.818 \cdot 10^{-21}$$

$$f = 1.85 \text{ GHz}$$

$$S = \frac{|\tilde{V}|_{\max}}{|\tilde{V}|_{\min}} = \frac{1 + |\Gamma|}{1 - |\Gamma|} = 2 \quad 2 - |\Gamma| = 1 + |\Gamma| \\ 1 = 3|\Gamma| \\ |\Gamma| = \frac{1}{3}$$

$$\text{VSWR} = 2$$

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{R_L + j\omega L_L + \frac{1}{j\omega C_L} - Z_0}{R_L + j\omega L_L + \frac{1}{j\omega C_L} + Z_0}$$

$$= \frac{j(w_2 L_L - \frac{1}{w_2 C_L})}{2Z_0 + j(w_2 L_L - \frac{1}{w_2 C_L})} \quad \begin{matrix} \text{Given from} \\ \text{the Discussion Session} \end{matrix}$$

$$|\Gamma| = \frac{|w_2 L_L - \frac{1}{w_2 C_L}|}{\sqrt{(2Z_0)^2 + (w_2 L_L - \frac{1}{w_2 C_L})^2}} = \frac{1}{3}$$

$C_L$  and  $L_L$

Solved by the Matlab

$$L_L = 13.87 \text{ nH}$$

$$C_L = 0.56 \text{ pF}$$